

# JEE Advanced 2019 - Paper 1 - Physics 12

Senan

## Problem [ Multiple Choice Multiple Correct ]

Two identical moving coil galvanometer have  $10\ \Omega$  resistance and full scale deflection at  $2\ \mu\text{A}$  current. One of them is converted into a Voltmeter of  $100\ \text{mV}$  full scale reading and the other into an Ammeter of  $1\ \text{mA}$  full scale current using appropriate resistors. These are then used to measure the voltage and current in the Ohm's law experiment with  $R = 1000\ \Omega$  resistor by using an ideal cell. Which of the following statement(s) is/are correct?

- (A) The resistance of the Voltmeter will be  $100\ \text{k}\Omega$ .
- (B) The resistance of the Ammeter will be  $0.02\ \Omega$  (round off to  $2^{\text{nd}}$  decimal places).
- (C) The measured value of  $R$  will be  $978\ \Omega < R < 982\ \Omega$ .
- (D) If the ideal cell is replaced by a cell having internal resistance of  $5\ \Omega$  then the measured value of  $R$  will be more than  $1000\ \Omega$ .

## What to Observe:

- Two identical moving coil galvanometers with resistance  $10\ \Omega$  and full scale deflection at  $2\ \mu\text{A}$ .
- One galvanometer is converted into a voltmeter with  $100\ \text{mV}$  full scale reading.
- The other galvanometer is converted into an ammeter with  $1\ \text{mA}$  full scale current.
- The voltmeter and ammeter are used to measure voltage and current in an Ohm's law experiment.
- The resistor used in the experiment has resistance  $R = 1000\ \Omega$ .
- The cell used is ideal.

## My Approach:

### Voltmeter

#### Thought

If I take the current through the created voltmeter as  $I_V$ , then the voltage across the galvanometer is given by:

$$V = I_V \cdot (R_G + R_S)$$

Since  $I_V = I_G$ , where  $I_G$  is the maximum current allowed by the galvanometer, we can rewrite the equation as:

$$V = I_G \cdot (R_G + R_S)$$



**Figure 1.** Circuit diagram showing a galvanometer with internal resistance  $R_G$  and a series resistance  $R_S$ , forming an voltmeter.

Given the voltage  $V = 100\ \text{mV} = 0.1\ \text{V}$  and the maximum current  $I_G = 2\ \mu\text{A} = 2 \times 10^{-6}\ \text{A}$ , the equivalent resistance  $R_{\text{eq}}$  is given by:

$$R_{\text{eq}} = \frac{V}{I_G} = \frac{0.1\ \text{V}}{2 \times 10^{-6}\ \text{A}} = 50,000\ \Omega = 50\ \text{k}\Omega$$

Therefore **Option A is incorrect.**

### Ammeter

#### Thought


The ammeter is created by connecting a galvanometer in parallel with a shunt resistance  $R_p$ . The current through the galvanometer is given by:

Let the equivalent resistance of the ammeter be  $R_A$ . The current through the ammeter,  $I_A$ , is related to the current through the galvanometer and the equivalent resistance as follows:

$$I_G R_G = I_A R_A$$

- $I_G$  is the current through the galvanometer.
- $R_G$  is the resistance of the galvanometer.

- $I_A$  is the total current through the ammeter.
- $R_A$  is the equivalent resistance of the ammeter.

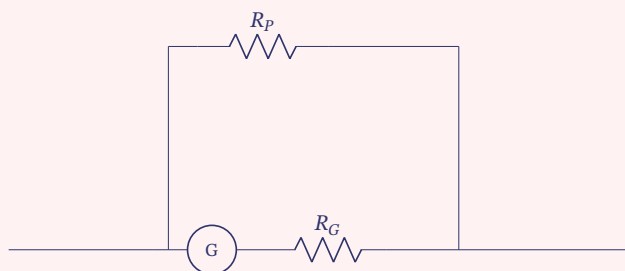

**Figure 2.** Circuit diagram showing a galvanometer with internal resistance  $R_G$  and a parallel shunt resistance  $R_P$ , forming an ammeter.

Given that  $I_G = 2 \mu\text{A} = 2 \times 10^{-6} \text{ A}$ ,  $R_G = 10 \Omega$ , and  $I_A = 1 \text{ mA} = 1 \times 10^{-3} \text{ A}$ , we can calculate the equivalent resistance  $R_A$  of the ammeter as follows:


$$R_A = \frac{I_G R_G}{I_A} = \frac{(2 \times 10^{-6} \text{ A}) \cdot 10 \Omega}{1 \times 10^{-3} \text{ A}} = 0.02 \Omega$$

Therefore **Option B is correct.**

### Ohm's Law Experiment

#### Thought

So, since Option C and Option D are referring to the measured value of  $R$ , let's solve it generally with an internal resistance  $r$  of the cell. For Option C, we can replace  $r$  with 0, and for Option D, we can replace  $r$  with  $5 \Omega$ .

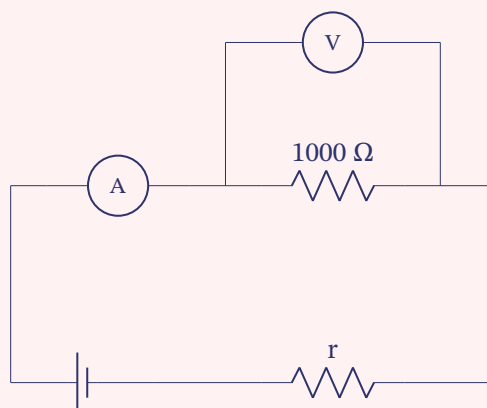

**Figure 3.** Circuit diagram showing a  $1000 \Omega$  resistor connected with a constructed ammeter and voltmeter, and a cell with internal resistance  $r$ .

Using KVL, taking the voltage across the cell as  $\varepsilon$  and the net current as  $I$ , we need to find  $\frac{V}{I} = R$ , where  $V$  is the reading in the voltmeter and  $I$  is the reading in the ammeter.

So, applying KVL in the loop, clockwise starting from the cell, we have:

$$\varepsilon - IR_A - V - Ir = 0$$

Now, divide by  $I$ :

$$\frac{\varepsilon}{I} - R_A - \frac{V}{I} - r = 0$$

So, since  $\frac{\varepsilon}{I} = R_{\text{eq}}$ , we can rewrite the equation for  $\frac{V}{I}$  as follows:

$$\frac{V}{I} = R_{\text{eq}} - R_A - r$$

We are given:

$$R_{\text{eq}} = R_A + \frac{1000 \Omega \times 50 \text{ k}\Omega}{50 \text{ k}\Omega + 1000 \Omega} + r$$

Then, the estimated resistance  $R_{\text{estimated}}$  is:

$$R_{\text{estimated}} = R_{\text{eq}} - R_A - r$$

Substitute  $R_{\text{eq}}$ :

$$R_{\text{estimated}} = \left( R_A + \frac{1000 \, \Omega \times 50 \, \text{k}\Omega}{50 \, \text{k}\Omega + 1000 \, \Omega} + r \right) - R_A - r$$

Simplifying:

$$R_{\text{estimated}} = \frac{1000 \, \Omega \times 50 \, \text{k}\Omega}{50 \, \text{k}\Omega + 1000 \, \Omega} \approx 980.39 \, \Omega$$

Therefore **Option C is correct**.

As the expression is independent of  $r$ , we can say that the measured value of  $R$  will be the same for any internal resistance of the cell. Therefore **Option D is incorrect**.

### Conclusion

Based on the detailed analysis and the computed expression for the estimated resistance  $R_{\text{estimated}}$ :

Options B, and C are correct.

Option A is incorrect because the resistance in the voltmeter calculated does not match the value stated in the option.

Option D is incorrect as the estimated value of  $R_{\text{estimated}}$  is independent of the internal resistance.

### Support the Channel:

If you found this explanation helpful and it helped you think like a JEE Advanced ranker, consider supporting the channel!

- **Subscribe** to *The Bored IITian* for more such high-quality JEE problem breakdowns.
- **Share it with 3 friends** who have **never heard of the channel**. Help them level up too!
- Drop a comment or suggestion - your feedback helps improve future content.

*Note from Senan:* The way I solve and explain problems in this PDF is simply how I personally approach and think through JEE questions. This is **not** the only way to solve them. What I'm sharing here is my mindset and thought process - use it as inspiration, not as a prescription. Develop your own flow, but always stay curious and logical!

**YouTube Channel:** [youtube.com/@bored\\_iitian](https://youtube.com/@bored_iitian)